
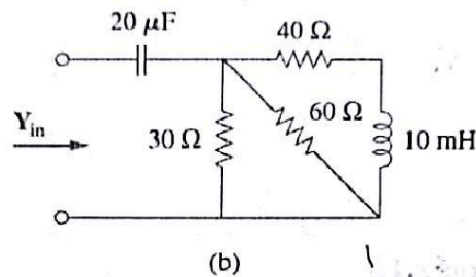


# VE215 2022Fall Assignment 5

Due Date: 23:59, Nov.27, 2022
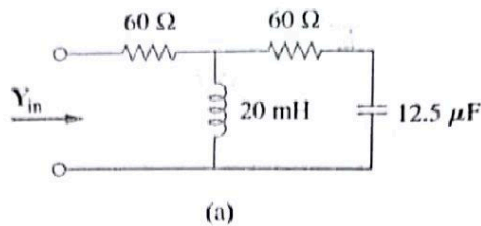
## Exercise 5.1 (20%)

Find the equivalent admittance of the circuits at  $\omega = 50 \text{ rad/s}$ .



$$(a) Z_L = j\omega L = j \times 50 \times 20 \times 10^{-3} = j\Omega \quad (\text{错}-2')$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 50 \times 12.5 \times 10^{-6}} = -1600j\Omega \quad (\text{错}-2')$$

$$\therefore Z = 60 + (j) \parallel (60 - 1600j) = (60 + j)\Omega \quad (\text{算} Z \text{ 对}-4')$$

$$\therefore Y_{in} = \frac{1}{Z} = \frac{1}{(60 + j)\Omega} = 0.0167 \angle -0.955^\circ \quad (10')$$


$$(b) Z_L = j\omega L = 0.5j \quad (\text{错}-2')$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 50 \times 20 \times 10^{-6}} = -1000j \quad (\text{错}-2')$$

$$\therefore Z = -1000j + 30 \parallel 60 \parallel (40 + 0.5j) = 13.334 - 999.944j \quad (\text{算} Z \text{ 对}-4')$$



$$\therefore Y_{in} = \frac{1}{Z} = \frac{1}{13.334 - 999.944j} = 1.333 \times 10^{-5} + 9.999 \times 10^{-4}j = 1 \times 10^{-4} \angle 89.236^\circ \quad (10')$$

$$(c) \Delta-Y:$$

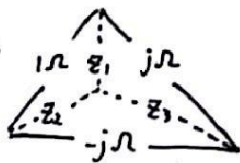


$$\therefore Z_1 = \frac{j}{1+j-j} = j\Omega, Z_2 = -j\Omega, Z_3 = 1\Omega \quad (\text{错}-3')$$
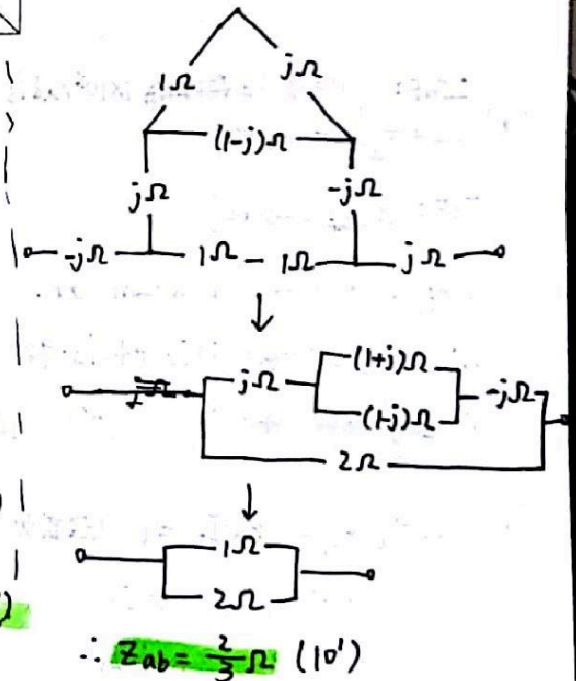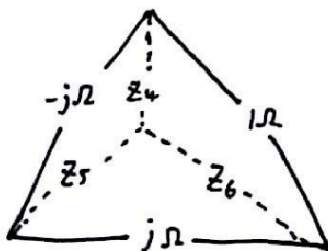
$$\therefore Z_4 = -j\Omega, Z_5 = 1\Omega, Z_6 = j\Omega \quad (\text{错}-3')$$




## Exercise 5.2 (20%)

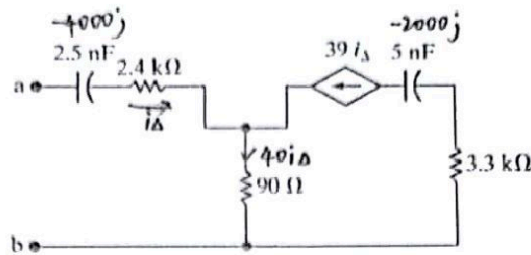(a) (15%) Calculate the Thevenin impedance between terminal a and b if the frequency of operation is  $(50/\pi)$  kHz.



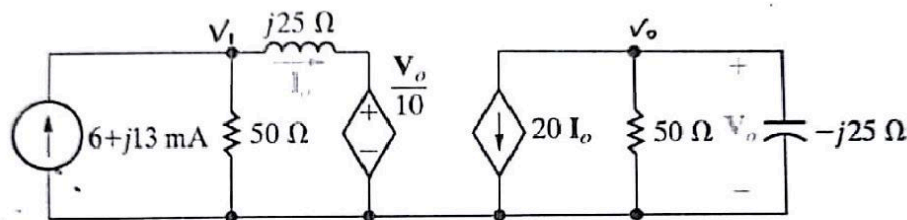(b) (15%) Find  $V_o$  and  $I_o$  shown in the figure below.



2.5 nF:  $\omega = 2\pi f = 1000 \times 10^3 \text{ rad/s}$

(a)  $Z_C = \frac{1}{j\omega C} = -4000j$

5 nF:  $Z_{C_{5nF}} = -2000j$

$\therefore$  Apply  $V_s = 1 \angle 0^\circ$  between ab.

$\therefore V_s = (2400 - 4000j)i_A + 40i_A \cdot 90 = (6000 - 4000j)i_A = 1 \angle 0^\circ$  (公式分 2')

$\therefore Z_{eq} = (6000 - 4000j) \Omega$  (15') (如果错了看公式吧, 算  $Z_{2.5nF}$ ,  $Z_{5nF}$  一个 2 分)

(b)  $\therefore \frac{V_o}{50} + \frac{V_o}{-25j} + 20I_o = 0$  (公式分 2')

$(2 + 4j)V_o = -2000I_o$

$V_o = (-200 + 400j)I_o$

$I_o = \frac{V_1 - \frac{V_o}{10}}{25j} \therefore V_1 = (-20 + 65j)I_o$


$\therefore 0.006 + 0.013j = \frac{V_1}{50} + I_o = (-0.4 + 1.3j)I_o + I_o = (0.6 + 1.3j)I_o$  (公式分 2')

$\therefore I_o = \frac{0.6 + 1.3j \times 10 \times 10^{-3}}{0.6 + 1.3j} = 10 \angle 0^\circ \text{ mA}$  ( $I_o$  7' 分)

$\therefore V_o = (-200 + 400j)I_o = -2 + 4j = 4.47 \angle 116.57^\circ \text{ V}$  (15')  
(8')  
 $\downarrow$   
 $V_o$



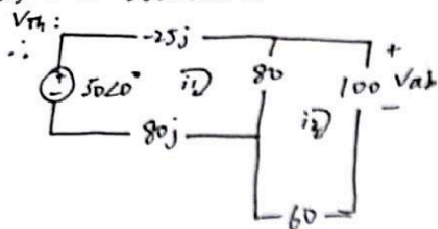(a)  $\omega = 2000 \text{ rad/s} \therefore Z_C = -25j \Omega, Z_L = 80j \Omega$  (2')




$$\therefore \begin{cases} (80 + j55)i_1 - 80i_2 = 50 \angle 0^\circ \\ 240i_2 - 80i_1 = 0 \end{cases}$$

$$\therefore i_2 = \frac{320}{2113} - \frac{370}{2113}j = 0.1514 - 0.1562j = 0.2175 \angle -45.88^\circ$$


$$\therefore V_{ab} = 21.755 \angle -45.88^\circ \text{ V} = (15.144 - 15.618j) \text{ V} = V_{Th} \text{ (10')}$$
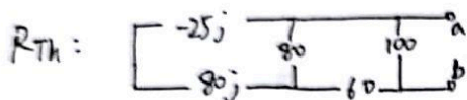
$$(V_{Th} = 21.755 \cos(2000t - 45.88^\circ) \text{ V 也行})$$




$$\therefore R_{Th} = 100 \parallel (60 + 80 \parallel 55j) = (48.237 + 10.4117j) \Omega \text{ (3')}$$

$$~~49.548 \angle 12.18^\circ~~$$

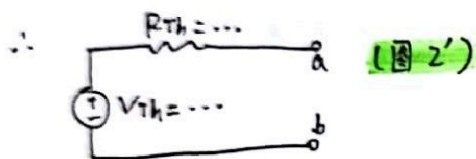

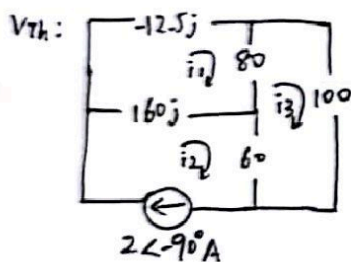$\omega = 4000 \text{ rad/s} \therefore Z_C = -12.5j \Omega, Z_L = 160j \Omega$  (2')




$$\therefore \begin{cases} (80 + 147.5j)i_1 - 160i_2 - 80i_3 = 0 \\ i_2 = 2 \angle -90^\circ \\ 240i_3 - 80i_1 - 60i_2 = 0 \end{cases}$$


$$\therefore i_3 = 1.178 \angle -82.62^\circ \text{ A} = (0.1513 - 1.1685j) \text{ A}$$

$$V_{Th} = V_{ab} = 100i_3 = 117.821 \angle -82.62^\circ \text{ V} = (15.13 - 116.85j) \text{ V} \text{ (10')}$$
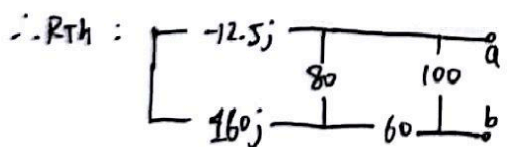
$$(V_{Th} = 117.821 \cos(4000t - 82.62^\circ) \text{ V 也行})$$


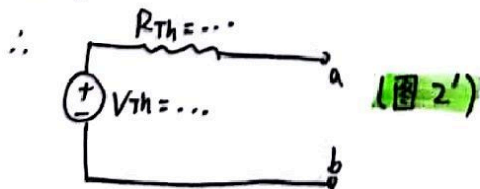
$$\therefore R_{Th} = 100 \parallel (60 + 80 \parallel 147.5j) = (55.9245 + 6.6620j) \Omega \text{ (3')}$$




来自 扫描全能王免费版

手机上的文档、证件扫描识别利器



扫描快速下载智能设备



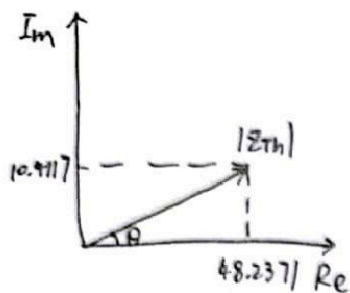

$$\therefore 1' \omega = 2000 \text{ rad/s}$$

$$\therefore R_{Th} = (48.2371 + 10.4117j) \Omega (= 49.348 \angle 12.18^\circ)$$

$$\therefore |Z_{Th}| = 49.348 \Omega, \theta = 12.18^\circ$$

(图上 Re, Im 坐标  $2 \times 1'$ )

$|Z_{Th}|$  值  $1'$

$\theta$  值  $1'$


图上有  $|Z_{Th}|$  和  $\theta$  标注  $1'$

$$2' \omega = 4000 \text{ rad/s}$$

$$\therefore R_{Th} = (55.9245 + 6.6620j) \Omega (= 56.3199 \angle 6.79^\circ)$$

$$\therefore |Z_{Th}| = 56.3199 \Omega, \theta = 6.79^\circ$$

(同上)

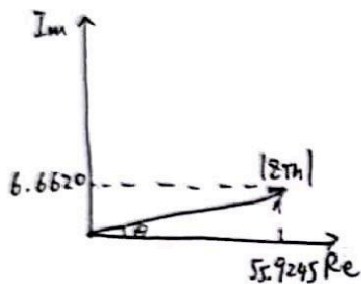

来自 扫描全能王免费版

手机上的文档、证件扫描识别利器



扫描快速下载智能设备