

VE215 2022Fall Assignment 1

Due Date: 23:59, , 2022

Exercise 1.1 (20%)

The voltage v (unit:V) across a device and the current i (unit:A) through it are

$$v(t) = 4e^{-t/2} \quad i(t) = \begin{cases} 0 & t < 0 \\ 5 \sin 3t & 0 \leq t < \frac{\pi}{6} \\ 5 & t \geq \frac{\pi}{6} \end{cases}$$

- (a) (10%) Calculate the total charge in the device at $t = 2$.
(b) (10%) Calculate the energy consumed by the device in the time period $3 \leq t \leq 5$.

$$\begin{aligned} (a) \quad q &= \int_{-\infty}^2 i dt = \int_0^{\frac{\pi}{6}} 5 \sin(3t) dt + \int_{\frac{\pi}{6}}^2 5 dt = -\frac{5}{3} \cos 3t \Big|_0^{\frac{\pi}{6}} + 5t \Big|_{\frac{\pi}{6}}^2 \\ &= \left(\frac{35}{3} - \frac{5\pi}{6} \right) C = 9.05 C \end{aligned}$$

$$\begin{aligned} (b) \quad E &= \int_3^5 v i dt = \int_3^5 4e^{-\frac{t}{2}} \cdot 5 dt = -40e^{-\frac{t}{2}} \Big|_3^5 \\ &= 40(e^{-\frac{3}{2}} - e^{-\frac{5}{2}}) J = 5.64 J \end{aligned}$$

for (a), considering the use of "through", $q=0$ is also acceptable.
if the answer is right, can give full points


VE215 2022Fall Assignment 1

Exercise 1.2 (35%)

In the circuit below, all the resistors have a resistance of R except the labeled one on the left bottom.

(a) (10%) Determine the number of branches, nodes, loops and meshes. Write your answers directly.

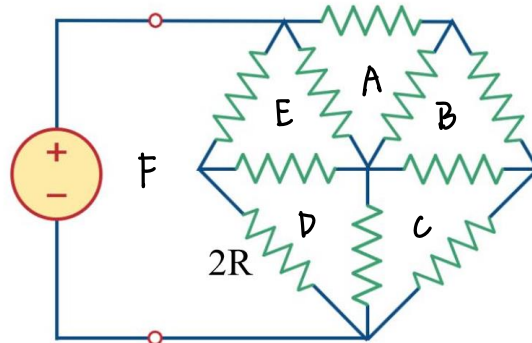(b) (25%) Calculate the equivalent resistance between the terminals.



(a) branch: 11, node: 6, mesh: 6 (each 2')

6 loops covering 1 area: A, B, C, D, E, F

7 loops covering 2 areas: AB, BC, CD, DE, EA, FE, FD

8 loops covering 3 areas: ABC, BCD, CDE, DEA, EAB, FEA, FED, FDC


9 loops covering 4 areas: ABCD, BCDE, CDEA, DEAB, EABC, FEAB, FDEA, FDEC, FDCB

4 loops covering 5 areas: ABUDE, FDEAB, FDEAC, FDECB


1 loop covering 6 areas: ABCDEF

Therefore, the number of loops is 35. (4')

(b)

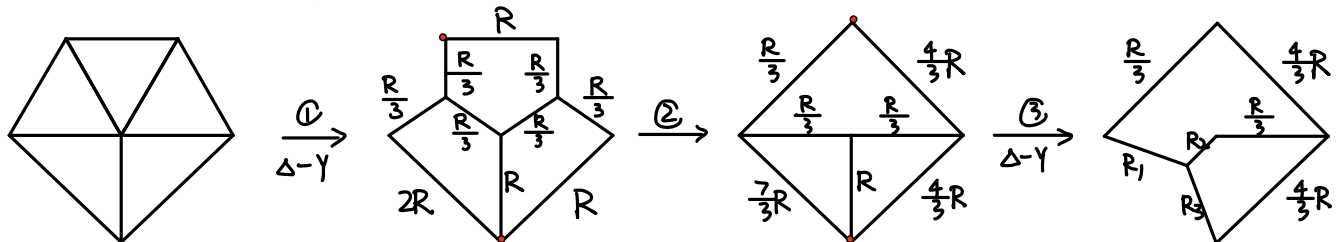
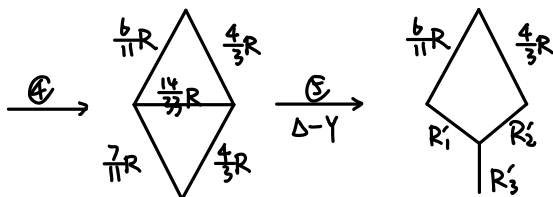
$$R_1 = \frac{\frac{R}{3} \cdot \frac{7}{3}R}{\frac{4}{3}R} = \frac{7}{33}R, \quad R_2 = \frac{\frac{R}{3} \cdot R}{\frac{4}{3}R} = \frac{1}{11}R, \quad R_3 = \frac{\frac{7}{3}R \cdot R}{\frac{4}{3}R} = \frac{7}{11}R$$



$$R_1' = \frac{\frac{7}{11}R \cdot \frac{14}{33}R}{\frac{7}{11}R} = \frac{98}{869}R, \quad R_2' = \frac{\frac{4}{3}R \cdot \frac{14}{33}R}{\frac{7}{11}R} = \frac{56}{237}R, \quad R_3' = \frac{\frac{7}{11}R \cdot \frac{4}{3}R}{\frac{7}{11}R} = \frac{28}{79}R$$

$$R_{eq} = \left(\frac{6}{11}R + R_1' \right) \parallel \left(\frac{4}{3}R + R_2' \right) + R_3' = \frac{9}{11}R \text{ (answer: 5')}$$


① ~ ⑤: each step 4'

Use other kind of transformation is also okay.

VE215 2022Fall Assignment 1

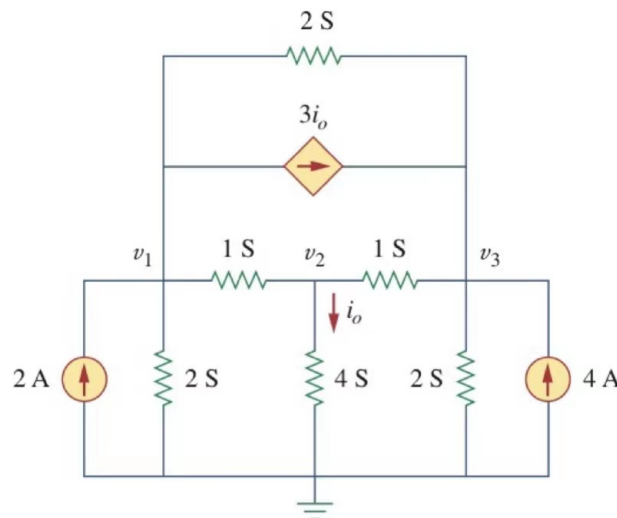Exercise 1.3 (30%)

Use nodal analysis to determine voltages v_1 , v_2 and v_3 in the circuit.



$$4V_2 = i_o$$

by KCL:
$$\begin{cases} 2 = 2V_1 + (V_1 - V_2) + 3i_o + 2(V_1 - V_3) \\ V_1 - V_2 = 4V_2 + (V_2 - V_3) \\ 2(V_1 - V_3) + 3i_o + (V_2 - V_3) + 4 = 2V_3 \end{cases}$$

right equation of KCL/inspection: 25'
one right equation: 10'
two right equation: 20'

We can solve that
$$\begin{cases} V_1 = \frac{19}{56} V \approx 0.339 V \\ V_2 = \frac{3}{8} V \approx 0.375 V \quad (5' \text{ for answer}) \\ V_3 = \frac{107}{56} V \approx 1.911 V \end{cases}$$

or by inspection: $G_{11} = 2 + 1 + 2 = 5S$, $G_{22} = 1 + 4 + 1 = 6S$, $G_{33} = 2 + 1 + 2 = 5S$

$$\begin{bmatrix} 5 & -1 & -2 \\ -1 & 6 & -1 \\ -2 & -1 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 2 - 3i_o \\ 0 \\ 3i_o + 4 \end{bmatrix}$$

$$4V_2 = i_o$$

$$\begin{bmatrix} 5 & -1 & -2 \\ -1 & 6 & -1 \\ -2 & -1 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 2 - 12V_2 \\ 0 \\ 12V_2 + 4 \end{bmatrix}$$


if mistake S as an unknown number and get answer of:
$$\begin{cases} V_1 = \frac{16}{5} S \\ V_2 = \frac{48}{11} S \\ V_3 = \frac{364}{55} S \end{cases}$$

5 points should be deducted.

VE215 2022Fall Assignment 1

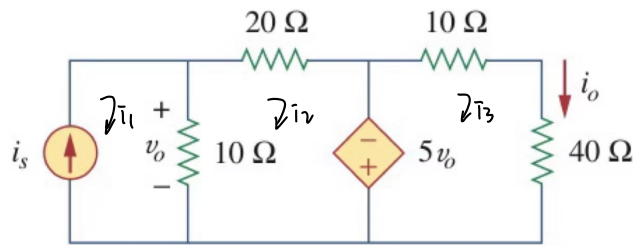Exercise 1.4 (15%)

Calculate the current gain i_o/i_s in the circuit.



Apply mesh analysis.

Obviously, $i_s = i_1$, $i_o = i_3$, $V_o = 10(i_1 - i_2) \Rightarrow i_1 = \frac{1}{10}V_o + i_2$

$$\text{By KVL: } \begin{cases} 20i_2 - 5V_o - V_o = 0 \Rightarrow i_2 = \frac{3}{10}V_o, i_1 = \frac{2}{5}V_o \\ 10i_3 + 40i_3 + 5V_o = 0 \Rightarrow i_3 = -\frac{1}{10}V_o \end{cases} \quad (10')$$

$$i_o/i_s = i_3/i_1 = -\frac{1/10}{2/5} = -\frac{1}{4} \quad (5')$$