


## VE215 2022Fall Assignment 8

Due Date: 23:59, Dec.11 ,2022

### Exercise 8.1 (30%)

For the circuit shown below, find the transfer function


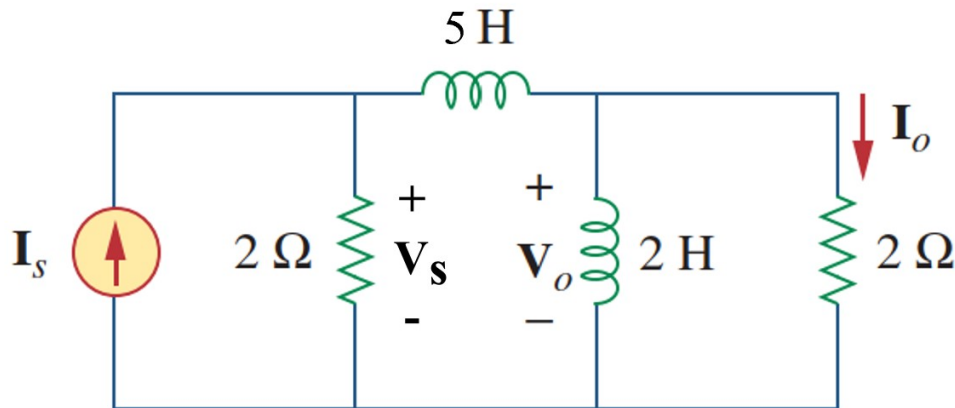
- (a) (15%)  $I_o(\omega)/I_s(\omega)$ , and its zeros and poles.
- (b) (15%)  $V_s(\omega)/I_s(\omega)$ , and its zeros and poles.



## VE215 2022Fall Assignment 8
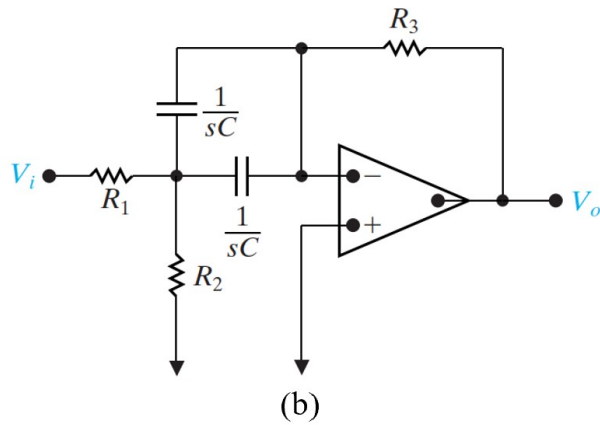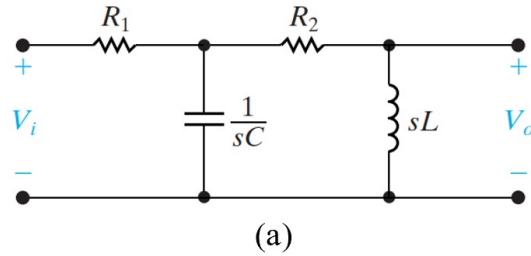
### Exercise 8.2 (30%)

Find  $H(s) = V_o(s)/V_i(s)$ , where  $s = j\omega$  in both circuits. Assume that  $R_1 = R_2 = R_3 = 100\Omega$ ,  $L = 1H$  and  $C = 1mF$  for (a) and (b),



## VE215 2022Fall Assignment 8


### Exercise 8.3 (40%)

Obtain the Bode plots ( $H - \omega$  and  $\psi - \omega$  relationship) for

$$(a) H(j\omega) = \frac{0.1(20 + j\omega)}{j\omega(5 + j\omega)}$$

$$(b) H(j\omega) = \frac{100(1 + j\omega)}{j\omega(-\omega^2 + 10j\omega + 25)}$$

(a)

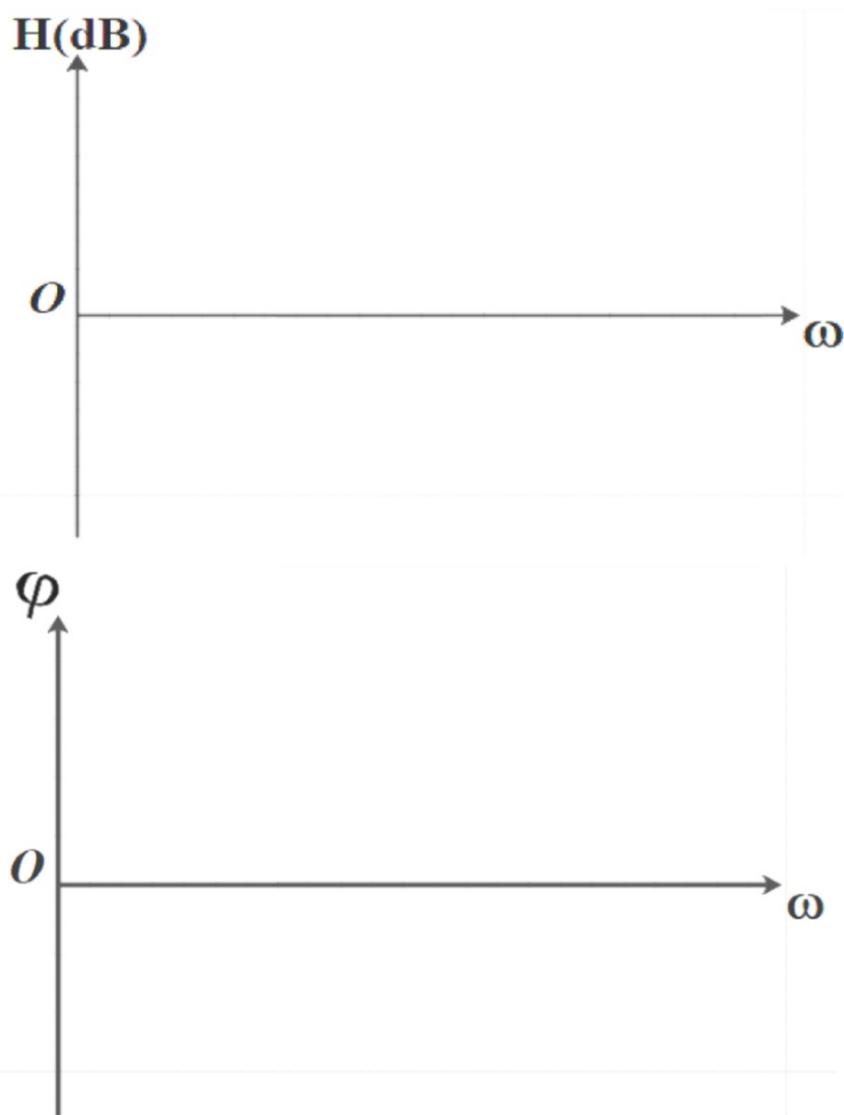

(b)

