

VE215 2022Fall Assignment 6

Due Date: 23:59, December 5th, 2022


In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

Exercise 6.1 (40%)

(a) For the given circuit, please calculate the total apparent power $|S|$, total real power P , total reactive power Q and the total power factor.

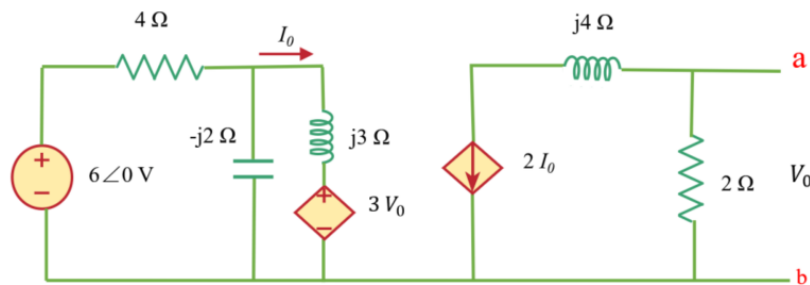(b) Suppose an impedance load Z_L is connected between a and b. Please calculate the value of Z_L that will absorb the maximum power and the value of that maximum power if


- Z_L is an impedance load
- Z_L is a pure resistance load



VE215 2022Fall Assignment 6

Exercise 6.2 (30%) Consider the power system shown below. Calculate:

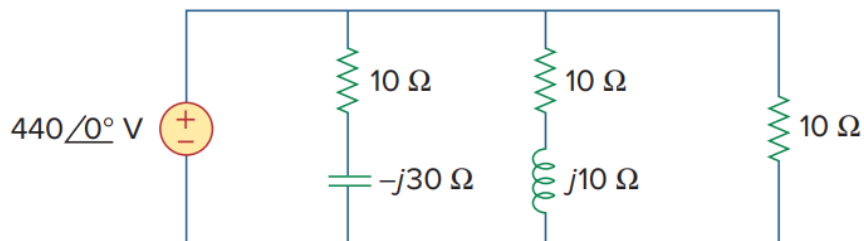- (a) the total complex power
- (b) the power factor
- (c) the parallel capacitance necessary to establish a unity power factor



VE215 2022Fall Assignment 6

Exercise 6.3 (30%)

Given the circuit below, calculate the equivalent impedance in each of the blocks. Also find I_o and the overall complex power supplied.

