

VE215 2022Fall Assignment 7

Due Date: 23:59, Dec.7th, 2022

In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

Exercise 7.1 (35%)

(a) (15%) A 480/2400-V rms step-up ideal transformer delivers 60 kW to a resistive load. Calculate: (1) the turns ratio (2) the primary current (3) the secondary current


$$(a) V_1 = 480 \text{ V}, V_2 = 2400 \text{ V}$$

$$(b) I_1 = \frac{60 \times 10^3}{480} = 125 \text{ A} \quad (5')$$

$$n = \frac{V_2}{V_1} = 5 \quad (5')$$

$$(c) I_2 = \frac{1}{n} I_1 = \frac{1}{5} I_1 = 25 \text{ A} \quad / I_2 = \frac{60 \times 10^3}{2400} = 25 \text{ A} \quad (5')$$

(b) (20%) Two linear transformers are cascaded as shown below. Calculate Z_{in} .

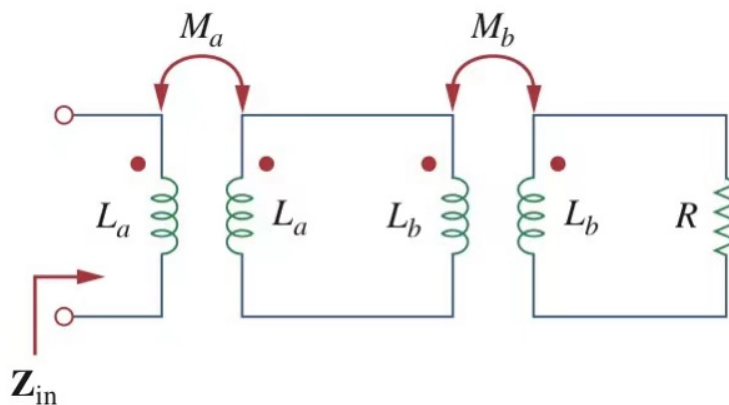

method 1: $Z_a = j\omega L_a$, $Z_b = j\omega L_b$

$$Z_{in} = \frac{V_{in}}{I_1}$$

$$\begin{cases} (R + Z_b)I_3 - j\omega M_b I_2 = 0 \Rightarrow I_3 = \frac{j\omega M_b}{R + Z_b} I_2 \\ (Z_a + Z_b)I_2 - j\omega M_b I_3 - j\omega M_a I_1 = 0 \Rightarrow I_2 = \frac{j\omega M_a}{Z_a + Z_b - j\omega M_b \frac{j\omega M_b}{R + Z_b}} I_1 = \frac{(R + Z_b) j\omega M_a}{(R + Z_b)(Z_a + Z_b) + \omega^2 M_b^2} I_1 \\ Z_a I_1 - j\omega M_a I_2 - V_{in} = 0 \Rightarrow V_{in} = Z_a I_1 - j\omega M_a I_2 = \left(Z_a + \frac{\omega^2 M_a^2 (R + Z_b)}{(R + Z_b)(Z_a + Z_b) + \omega^2 M_b^2} \right) I_1 \end{cases}$$

(5' for each KVL equation)


$$Z_{in} = Z_a + \frac{\omega^2 M_a^2 (R + Z_b)}{(R + Z_b)(Z_a + Z_b) + \omega^2 M_b^2}$$

$$= j\omega L_a + \frac{\omega^2 M_a^2 (R + j\omega L_b)}{j\omega R(L_a + L_b) - \omega^2 (L_a L_b + L_b^2 - M_b^2)}$$

$$= j\omega L_a + \frac{\omega^2 M_a^2}{j\omega (L_a + L_b) + \frac{\omega^2 M_b^2}{j\omega L_b + R}} / j\omega L_a - \frac{j\omega M_a^2}{j\omega (L_a + L_b) - \frac{j\omega M_b^2}{j\omega L_b + R}} \quad (\text{most students may have this answer})$$

$$= \frac{\omega^2 R(L_a^2 + L_a L_b - M_a^2) + j\omega^3 (L_a^2 L_b + L_a L_b^2 - L_a M_b^2 - L_b M_a^2)}{\omega^2 (L_a L_b + L_b^2 - M_b^2) - j\omega R(L_a + L_b)} \quad (5' for the answer)$$

method 2: use T-transformation

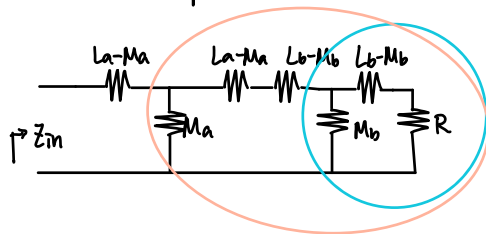


(equivalent circuit: 5')

$$\begin{aligned} Z_1 &= j\omega M_b \parallel [R + j\omega(L_b - M_b)] \\ &= \frac{j\omega M_b (R + j\omega L_b - j\omega M_b)}{j\omega L_b + R} = j\omega M_b - \frac{j\omega M_b}{j\omega L_b + R} \quad (5') \end{aligned}$$

$$\begin{aligned} Z_2 &= [Z_1 + j\omega(L_a - M_a) + j\omega(L_b - M_b)] \parallel (j\omega M_a) \\ &= \frac{j\omega M_a [Z_1 + j\omega(L_a - M_a) + j\omega(L_b - M_b)]}{Z_1 + j\omega L_a + j\omega(L_b - M_b)} \\ &= \frac{j\omega M_a [j\omega(L_a L_b - M_a M_b) + \frac{j\omega M_b (R + j\omega L_b - j\omega M_b)}{j\omega L_b + R}]}{j\omega(L_a L_b - M_b) + \frac{j\omega M_b (R + j\omega L_b - j\omega M_b)}{j\omega L_b + R}} \\ &= \frac{j\omega M_a [j\omega(L_a L_b) - j\omega M_a - \frac{j\omega M_b}{j\omega L_b + R}]}{j\omega(L_a L_b) - \frac{j\omega M_b}{j\omega L_b + R}} \quad (5') \end{aligned}$$

$$\begin{aligned} Z_{in} &= Z_2 + j\omega(L_a - M_a) \\ &= j\omega(L_a - M_a) + \frac{j\omega M_a [j\omega(L_a L_b - M_a M_b) + \frac{j\omega M_b (R + j\omega L_b - j\omega M_b)}{j\omega L_b + R}]}{j\omega(L_a L_b - M_b) + \frac{j\omega M_b (R + j\omega L_b - j\omega M_b)}{j\omega L_b + R}} \\ &= \frac{\omega^2 R(L_a^2 + L_a L_b - M_a^2) + j\omega^3(L_a^2 L_b + L_a L_b^2 - L_a M_b^2 - L_b M_a^2)}{\omega^2(L_a L_b + L_b^2 - M_b^2) - j\omega R(L_a + L_b)} \quad (5) \end{aligned}$$

method 3:

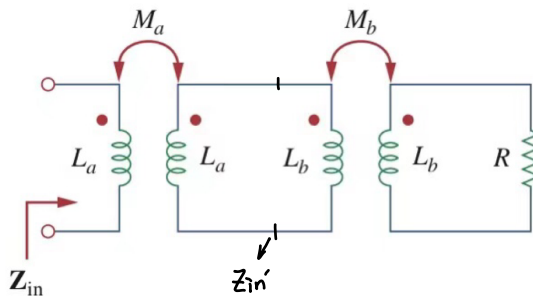

$$Z_{in}' = j\omega L_b + \frac{\omega^2 M_b^2}{j\omega L_b + R} \quad (10')$$

$$Z_{in} = j\omega L_a + \frac{\omega^2 M_a^2}{j\omega L_a + j\omega L_b + \frac{\omega^2 M_b^2}{j\omega L_b + R}} \quad (10')$$


right answer: full points

Since there're many methods, each right step worths 5'

VE215 2022Fall Assignment 7

Exercise 7.2 (25%)

Find current I_0 in the circuit.

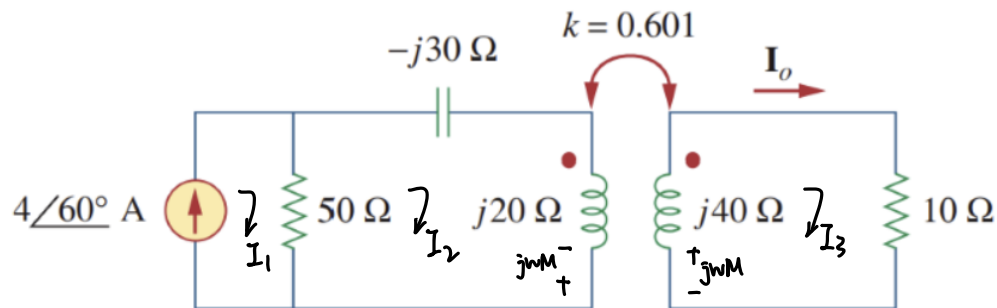

$$k = \frac{M}{\sqrt{L_1 L_2}} = 0.601$$

$$M = 0.601 \sqrt{L_1 L_2}$$

$$j\omega M = 0.601 j\omega \sqrt{L_1 L_2} = 0.601 \sqrt{20 \times 40} = 17.00 j \text{ V} \quad \text{get right } j\omega M: 10'$$

$$I_1 = 4 \angle 60^\circ \text{ A}, I_0 = I_3$$

$$\text{by KVL: } (-j30 + j20)I_2 - j\omega M I_3 + 50(I_2 - I_1) = 0 \quad (5')$$

$$10I_3 - j\omega M I_2 + 40jI_3 = 0 \quad (5')$$

$$(50 - 10j)I_2 - 17.00jI_3 = 50I_1 = 200 \angle 60^\circ$$

$$-17.00jI_2 + (10 + 40j)I_3 = 0$$

$$\Delta = \begin{vmatrix} 50 - 10j & -17j \\ -17j & 10 + 40j \end{vmatrix} = (50 - 10j)(10 + 40j) + 289 = 1189 + j1900$$

$$\Delta_2 = \begin{vmatrix} 50 - 10j & 200 \angle 60^\circ \\ -17j & 0 \end{vmatrix} = 3400 \angle 150^\circ$$

$$I_0 = I_3 = \frac{\Delta_2}{\Delta} = -0.0539 + j1.516$$


$$= 1.52 \angle 92.04^\circ \text{ A} \quad (5')$$

VE215 2022Fall Assignment 7

Exercise 7.3 (40%)

For the ideal transformer circuit below, find:

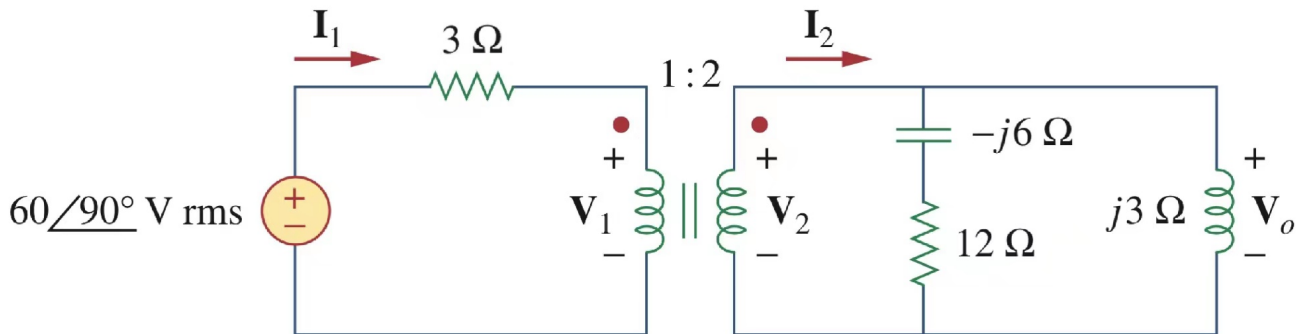- (a) I_1 and I_2
- (b) V_1 and V_2
- (c) the complex power supplied by the source



$$(a) \quad \frac{V_2}{V_1} = n = \frac{I_1}{I_2} = 2 \quad (5')$$

$$Z_R = \frac{(-j6 + 12) \parallel j3}{2^2} = \frac{3}{17} + j\frac{27}{34} = 0.176 + j0.794 \, \Omega \quad (5')$$

$$I_1 = \frac{60 \angle 90^\circ}{3 + Z_R} = \frac{40}{9} + j\frac{160}{9} = 4.44 + j17.78 \, \text{A} = 18.32 \angle 75.97^\circ \, \text{A} \quad (5')$$

$$I_2 = \frac{I_1}{2} = \frac{20}{9} + j\frac{80}{9} = 2.22 + j8.89 \, \text{A} = 9.16 \angle 75.97^\circ \, \text{A} \quad (5')$$

$$(b) \quad 3I_1 + V_1 - 60 \angle 90^\circ = 0 \Rightarrow V_1 = -\frac{40}{3} + j\frac{20}{3} = -13.33 + j6.67 \, \text{V} = 14.91 \angle 153.43^\circ \, \text{V} \quad (5')$$

$$V_2 = 2V_1 = -\frac{80}{3} + j\frac{40}{3} = -26.67 + j13.33 \, \text{V} = 29.82 \angle 153.43^\circ \, \text{V} \quad (5')$$

$$(c) \quad S = V_s I_1^* = 60 \angle 90^\circ \cdot \left(\frac{40}{9} - j\frac{160}{9} \right) \quad (5') \quad (\text{rms value!})$$

$$= \frac{3200}{3} + j\frac{800}{3} = 1066.67 + j266.67 \, \text{VA} = 1099.49 \angle 14.04^\circ \, \text{VA} \quad (5')$$