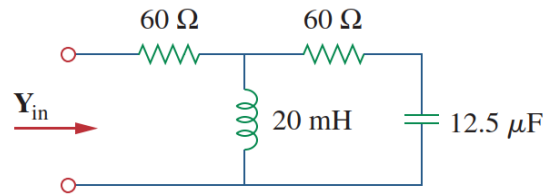


VE215 2022Fall Assignment 5


Due Date: 23:59, Nov.27 ,2022

Exercise 5.1 (30%)


- (a) Find the equivalent admittance of the circuits at $\omega = 50 \text{ rad/s}$.
- (b) Find the equivalent admittance of the circuits at $\omega = 50 \text{ rad/s}$.
- (c) Find the equivalent impedance Z_{ab} .



(a)

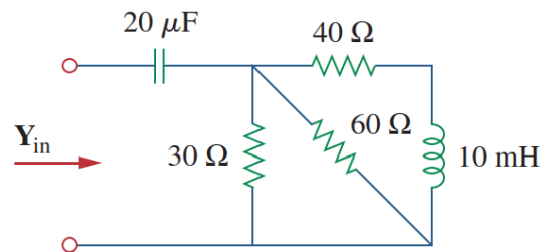

(b)

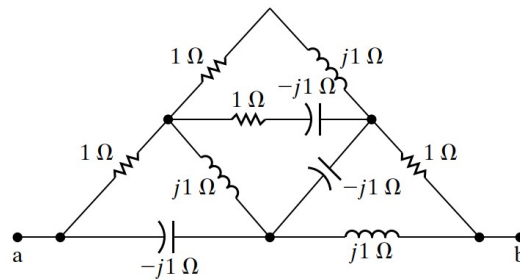


(c)


VE215 2022Fall Assignment 5

Exercise 5.2 (30%)

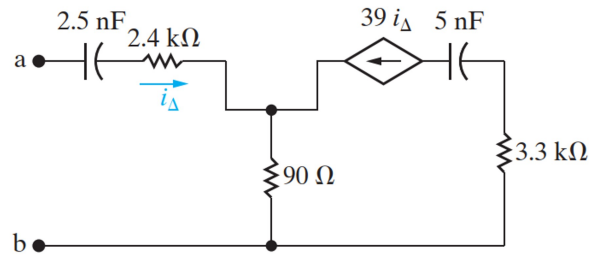(a) (15%) Calculate the Thevenin impedance between terminal a and b if the frequency of operation is $(50/\pi)$ kHz.



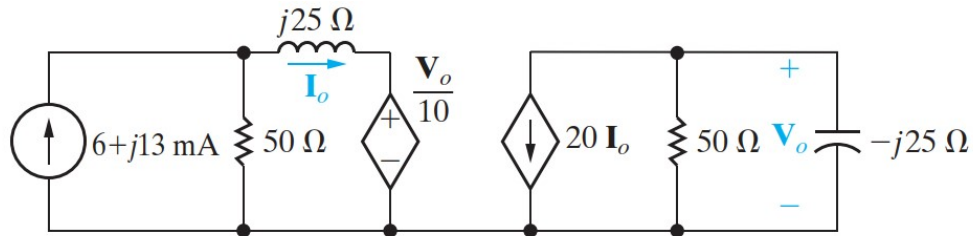(b) (15%) Find V_o and I_o shown in the figure below.



VE215 2022Fall Assignment 5

Exercise 5.3 (40%)

(a) (30%) Please find the Thevenin equivalent circuits between terminal a and b under $\omega = 2000\text{rad/s}$ and $\omega = 4000\text{rad/s}$.

(Hint: Consider whether to turn on or turn off the voltage source and current source based on the frequency you choose.)

(b) (10%) Please draw two phasor diagrams of the two Thevenin equivalent impedances under two frequencies ($\omega = 2000\text{rad/s}$ and $\omega = 4000\text{rad/s}$).

