


VE215 2022Fall Assignment 2

Due Date: 23:59, October 17th, 2022

3.26.

Exercise 2.1 (45%)

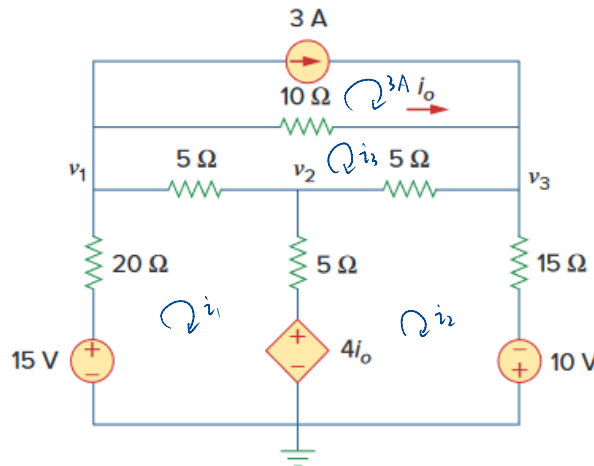- (a) (15%) Calculate v_1 , v_2 and v_3 in the following circuit using Nodal Analysis.
 (b) (15%) Calculate i_0 in the following circuit using Mesh Analysis.
 (c) (15%) Verify your result of i_0 by applying Superposition rule.



公式分差不多就给满吧!

$$(a) \begin{cases} \frac{v_1 - 15}{20} + \frac{v_1 - v_2}{5} + i_0 + 3 = 0 \\ \frac{v_2 - v_1}{5} + \frac{v_2 - v_3}{5} + \frac{v_2}{5} = 0 \\ \frac{v_3 - v_2}{5} + \frac{v_3 + 10}{15} - i_0 - 3 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} i_0 = \frac{v_1 - v_3}{10} \quad (10\%) \\ v_1 = -7.19 \text{ V} \\ v_2 = -2.78 \text{ V} \\ v_3 = 2.89 \text{ V} \\ i_0 = -1.01 \text{ A} \quad (5\%) \end{cases}$$

$$(b) \begin{cases} -15 + 20i_1 + 5(i_1 - i_2) + 5(i_2 - i_3) + 4i_0 = 0 \\ -4i_0 + 5(i_2 - i_1) + 5(i_2 - i_3) + 15i_2 - 10 = 0 \\ 5(i_3 - i_1) + 10(i_3 - 3) + 5(i_3 - i_2) = 0 \\ i_0 = i_3 - 3 \end{cases} \quad (10\%)$$

$$\Rightarrow \begin{cases} i_1 = 1.11 \text{ A} \\ i_2 = 0.86 \text{ A} \\ i_3 = 1.99 \text{ A} \\ i_0 = -1.01 \text{ A} \quad (5\%) \end{cases}$$

(c) 15V:

$$\begin{cases} \frac{v_1 - 15}{20} + \frac{v_1 - v_2}{5} + i_0 = 0 \\ \frac{v_2 - v_1}{5} + \frac{v_2 - 4i_0}{5} + \frac{v_2 - v_3}{5} = 0 \\ \frac{v_3 - v_2}{5} + \frac{v_3}{15} - i_0 = 0 \end{cases}$$

$$i_0 = \frac{v_1 - v_3}{10} \quad (5\%)$$

Current source:

$$\begin{cases} \frac{v_1 - v_2}{5} + 3 + i_0 + \frac{v_1}{20} = 0 \\ \frac{v_2 - v_1}{5} + \frac{v_2 - 4i_0}{5} + \frac{v_2 - v_3}{5} = 0 \\ -i_0 - 3 + \frac{v_3 - v_2}{5} + \frac{v_3}{15} = 0 \end{cases}$$

$$i_0 = \frac{v_1 - v_3}{10} \quad (5\%)$$

-10V:

$$\begin{cases} \frac{v_1}{20} + \frac{v_1 - v_2}{5} + i_0 = 0 \\ \frac{v_2 - v_1}{5} + \frac{v_2 - 4i_0}{5} + \frac{v_2 - v_3}{5} = 0 \\ \frac{v_3 - v_2}{5} + \frac{v_3 + 10}{15} - i_0 = 0 \end{cases}$$

$$i_0 = \frac{v_1 - v_3}{10} \quad (5\%)$$

$$i_{01} = 0.176 \text{ A} \quad \left(\frac{90}{511}\right)$$

$$i_{02} = 0.137 \text{ A} \quad \left(\frac{10}{73}\right)$$

$$i_{03} = -1.32 \text{ A} \quad \left(-\frac{675}{511}\right)$$

用了 superposition 就行, 不一定要三个.


$$i_0 = -1.01 \text{ A}$$

VE215 2022Fall Assignment 2


4.55

Exercise 2.2 (35%)

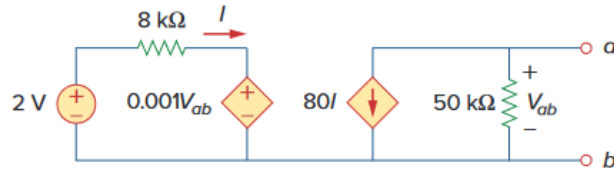- (a) (20%) Obtain the Norton equivalent circuit at the terminal a-b. Draw the circuit.
 (b) (10%) Calculate the voltage V_{ab} if now a resistor of $10k\Omega$ connects between terminal a-b.
 (c) (10%) Calculate the maximum power transferred to a resistor that connects between terminal a-b. Also calculate the resistance of that resistor.




(a)

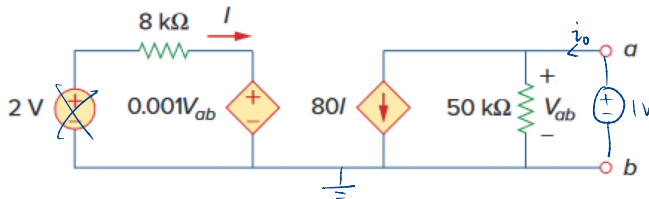

$$\begin{cases} I_0 = 80I + \frac{1}{50k} \\ I = -\frac{0.001}{8k} \end{cases}$$

$$I_0 = 1 \times 10^{-5} \text{ A}$$

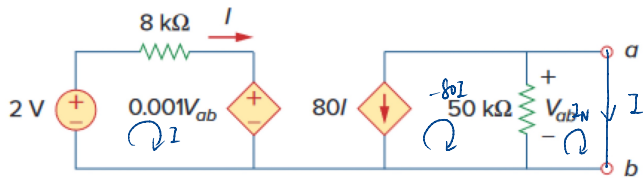
$$R_{eq} = \frac{1}{I_0} = 1 \times 10^5 \Omega \quad (5\%)$$



$$\begin{aligned} -2 + 8k \cdot I + 0.001 V_{th} &= 0 \\ V_{th} &= -80I \cdot 50k \\ V_{th} &= -2000 \text{ V} \end{aligned}$$


$$\begin{cases} V_{ab} = (-80I - I_N) \cdot 50k \\ -2 + 8k \cdot I + 0.001 V_{ab} = 0 \\ I_N = -80I \end{cases}$$
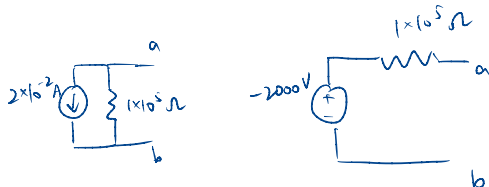
$$I_N = -2 \times 10^{-2} \text{ A} \quad (10\% \text{ I 方向对错了}) \quad V_{th} = -2000 \text{ V} \quad (10\% \text{ V 方向对错了}) \quad (10\%)$$



(5%)

(b)

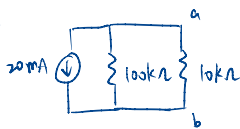

$$V_{ab} = -181.8 \text{ V} \quad (5\%)$$

正负 -2

(c)


$$R = 100k\Omega \quad (5\%)$$

$$P = (10mA)^2 \times 100k\Omega = 10 \text{ W} \quad (5\%)$$

Q.69

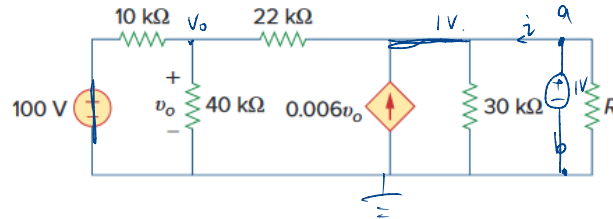Exercise 2.3 (20%)

Calculate the maximum power that can be delivered to the variable resistor R in the following circuit.



R_{Th} :

$$\begin{cases} \frac{v_o}{10k} + \frac{v_o}{40k} + \frac{v_o - 1}{22k} = 0 \\ \frac{1 - v_o}{22k} - 0.006v_o + \frac{1}{30k} - i = 0 \end{cases}$$

$$i = -0.00153 \text{ A}$$

$$R_{Th} = \frac{1}{i} = -652 \Omega < 0 \quad (15\%)$$

$$P = +\infty \quad (5\%)$$