

VE215 2022Fall Assignment 7

Due Date: 23:59, Dec.7th, 2022


In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

Exercise 7.1 (35%)

(a) (15%) A 480/2400-V rms step-up ideal transformer delivers 60 kW to a resistive load.

Calculate: (1) the turns ratio (2) the primary current (3) the secondary current

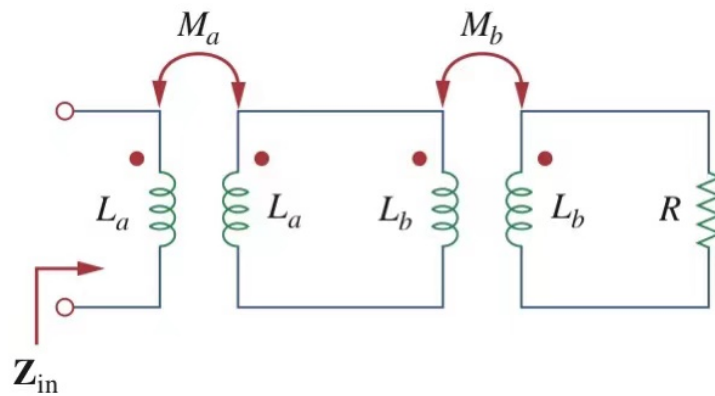
(b) (20%) Two linear transformers are cascaded as shown below. Calculate Z_{in} .



VE215 2022Fall Assignment 7

Exercise 7.2 (25%)

Find current I_0 in the circuit.

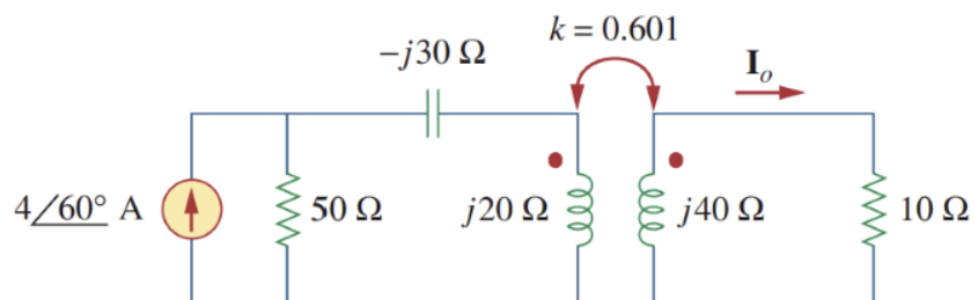

VE215 2022Fall Assignment 7

Exercise 7.3 (40%)

For the ideal transformer circuit below, find:

- (a) I_1 and I_2
- (b) V_1 and V_2
- (c) the complex power supplied by the source

