


VE215 2022Fall Assignment 4

Due Date: 23:59, November 6th, 2022

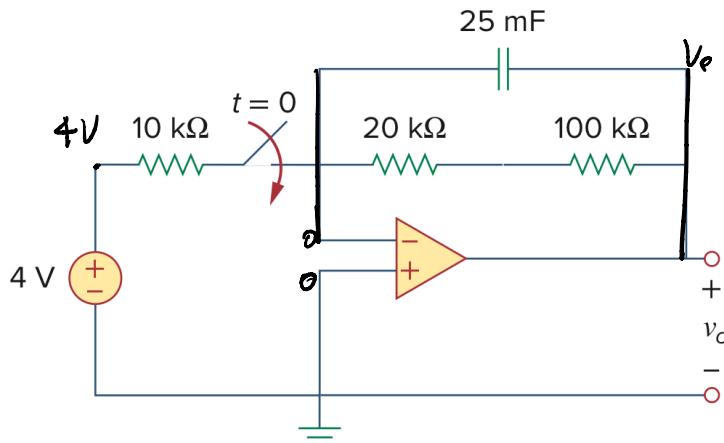Exercise 4.1 (25%)

The following figure shows a op-amp circuit. The switch is closed at $t=0$.

- (10%) Derive the differential equation that relates to the output voltage v_o .
- (15%) Derive $v_o(t)$ of $t > 0$.



(a) At $t \leq 0$ $v_o(t) = 0$ (Not a must)

At $t > 0$ $\frac{0-4}{10k\Omega} + \frac{0-v_o}{120k\Omega} + (-25 \times 10^{-3} F \times \frac{dv_o}{dt}) = 0$ 5'

Hence
$$\frac{dv_o}{dt} + \frac{v_o}{3000} + \frac{2}{125} = 0$$
 5'

(b) At $t=0$, $v_o(0^-) = v_o(0^+) = 0$ 2'

At $t=\infty$, $\frac{dv_o}{dt}(\infty) = 0$, According to the differential equation ($t>0$)

$\Rightarrow v_o(\infty) = -48V$ 3'

$v_o(t) = (A e^{-\frac{t}{3000}} + B)v$ 5'

$v_o(\infty) = -48V \Rightarrow B = -48$

$v_o(0^-) = v_o(0^+) = 0$, $A+B=0 \Rightarrow A=48$


Hence $v_o(t) = 48(e^{-\frac{t}{3000}} - 1)v$ for $t > 0$. 5'

VE215 2022Fall Assignment 4

Exercise 4.2 (25%)

For the op-amp circuit shown below, the switch is connected to the branch connected with a 3Ω resistor and a $24V$ independent voltage source at $t < 0$, and it is switched to the branch connected with a 8Ω resistor and a $20V$ independent voltage source at $t \geq 0$.

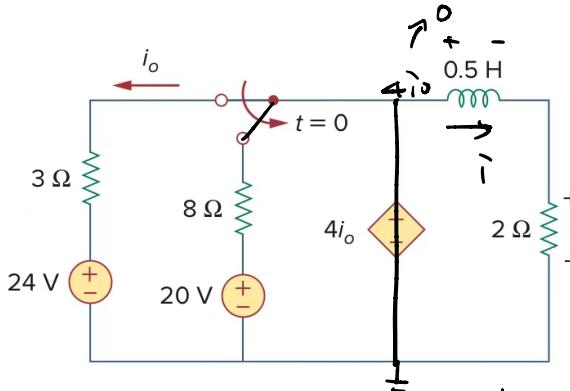- (a) (10%) Find $v(t)$ for $t < 0$.
- (b) (15%) Find $v(t)$ for $t \geq 0$.



(a) At $t < 0$ steady state. \Rightarrow inductor as a wire.

$$i_o = \frac{4i_o - 24V}{3\Omega} \Rightarrow i_o = 24A \quad 5'$$

$$v(t) = 4i_o = 96V \quad \text{for } t < 0 \quad 5'$$

(b) At $t > 0$

$$\text{At } t=0 \quad v(0^-) = v(0^+) = 96V$$

$$\text{At } t>0 \quad i_o = 0A.$$

Hence the branch with $4i_o$ dependent source is treated as a wire.

$$\angle \frac{di(t)}{dt} + 2i(t) = 0, L = 0.5H \quad 5'$$

$$\text{Hence } \frac{di(t)}{dt} + 4i(t) = 0 \Rightarrow i(t) = Ae^{-4t} \quad 5'$$

$$\text{with } v(0) = v(0^+) = 96V \Rightarrow i(0^-) = i(0^+) = \frac{96V}{2\Omega} = 48A$$

$$\text{Hence } A = 48$$


$$\Rightarrow i(t) = 48e^{-4t} A$$

$$v(t) = 2i(t) = 96e^{-4t} V \quad \text{for } t > 0 \quad 5'$$

VE215 2022Fall Assignment 4

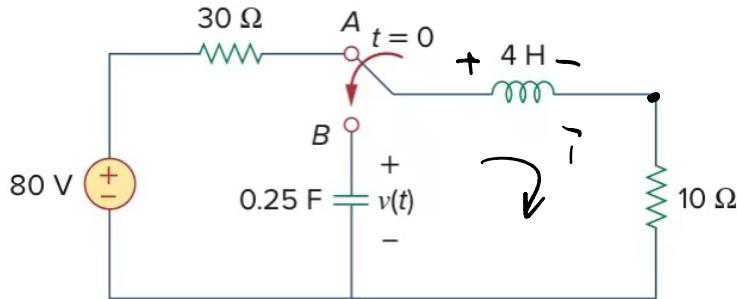Exercise 4.3 (20%)

The switch in the following figure moves from position A to position B at $t = 0$ (please note that the switch must connect to point B before it breaks the connection at A, a make-before-break switch). Let $v(0) = 0V$, find $v(t)$ for $t > 0$.



At $t < 0$

steady state \rightarrow inductor as a wire

$$i(t) = \frac{80V}{(30+10)\Omega} = 2A \quad 3'$$

$$\text{At } t > 0 \quad i(0^-) = i(0^+) = 2A, \quad V(0^-) = V(0^+) = 0V. \quad 1'$$

$$i(t) = -C \frac{dv(t)}{dt} \quad 3'$$

$$10i - v(t) + L \frac{di(t)}{dt} = 0 \quad 3'$$

$$\Rightarrow -L \frac{d^2v(t)}{dt^2} - 10C \frac{dv(t)}{dt} - v(t) = 0 \quad L = 4H, \quad C = 0.25F$$

$$\Rightarrow \frac{d^2v(t)}{dt^2} + 2.5 \frac{dv(t)}{dt} + v(t) = 0 \quad 5'$$

$$\text{with } s^2 + 2.5s + 1 = 0 \Rightarrow s_1 = -2, \quad s_2 = -\frac{1}{2}$$

$$\text{Hence } v(t) = Ae^{-2t} + Be^{-\frac{1}{2}t}$$

$$v(0) = v(0^+) = 0V$$

$$\frac{dv(0)}{dt} = -\frac{i(0)}{C} = -8$$


$$\left\{ \begin{array}{l} A + B = 0 \\ -2A - \frac{1}{2}B = -8 \end{array} \right. \Rightarrow \left\{ \begin{array}{l} A = \frac{16}{3} \\ B = -\frac{16}{3} \end{array} \right.$$

$$\text{Hence } v(t) = \frac{16}{3} (e^{-2t} - e^{-\frac{1}{2}t})V \quad \text{for } t > 0 \quad 4'$$


VE215 2022Fall Assignment 4

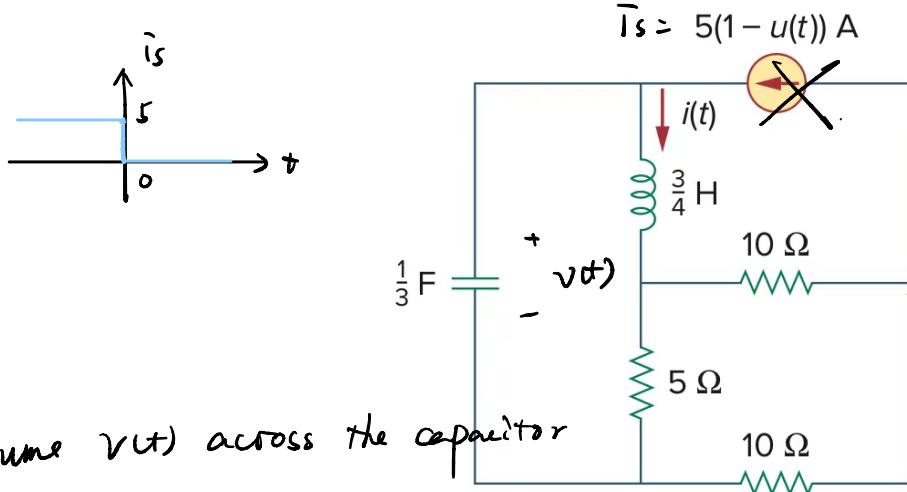Exercise 4.4 (30%)

The input current source of the following circuit is $5(1 - u(t))\text{A}$. Please find $i(t)$ for $t > 0$.




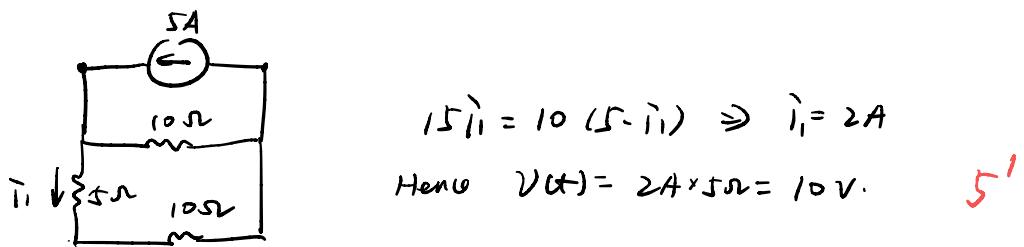At $t \leq 0$ $i_s = 5\text{A}$ steady state \rightarrow capacitor cut-off. Inductor as wire



At $t > 0$ $v(0^-) = v(0^+) = 10\text{V}$, $i(0^-) = i(0^+) = 5\text{A}$. 5'

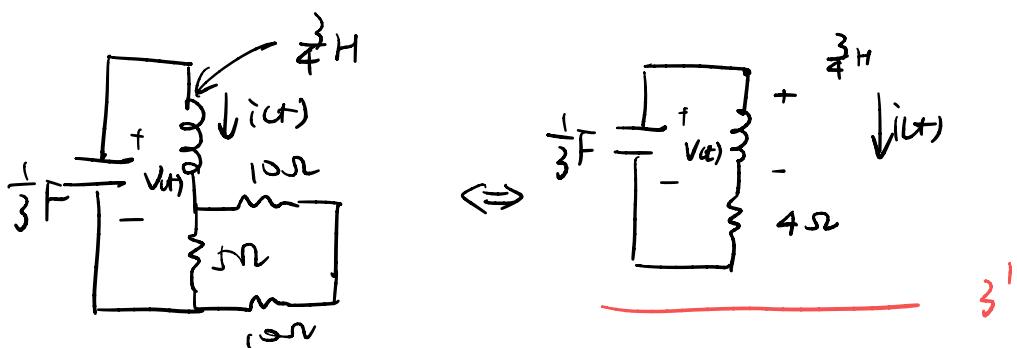$i_s = 0\text{A} \Leftrightarrow$ the current source cut-off



$$L \frac{di(t)}{dt} + i(t) \cdot 4\Omega - v(t) = 0 \quad 5'$$

$$i(t) = -C \frac{dv(t)}{dt} \Rightarrow v(t) = -\frac{1}{C} \int_0^\infty i(t) dt \quad \left. \begin{array}{l} \Rightarrow L \frac{di(t)}{dt} + 4i(t) + \frac{1}{C} \int_0^\infty i(t) dt = 0 \\ \downarrow \text{differentiate by } t \end{array} \right.$$

$$L \frac{d^2i(t)}{dt^2} + 4 \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$$


$$\Rightarrow L \frac{d^2i(t)}{dt^2} + \frac{16}{3} \frac{di(t)}{dt} + 4i(t) = 0 \quad 5' \Rightarrow s^2 + \frac{16}{3}s + 4 = 0 \Rightarrow s_1 = \frac{-8+2\sqrt{7}}{3}, s_2 = \frac{-8-2\sqrt{7}}{3}$$

$$\text{Hence } i(t) = Ae^{\frac{-8+2\sqrt{7}}{3}t} + Be^{\frac{-8-2\sqrt{7}}{3}t} \quad A \quad 3' \quad \text{2 next page}$$

VE215 2022Fall Assignment 4

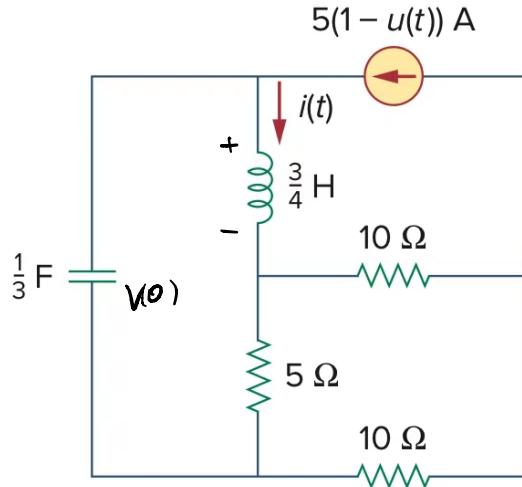Exercise 4.4 (30%)

The input current source of the following circuit is $5(1 - u(t))\text{A}$. Please find $i(t)$ for $t > 0$.



(continue)

with initial condition: $V(0) = 10\text{V}$, $i(0) = 5\text{A}$

$$V(0) = L \frac{di(0)}{dt} + 4i(0)$$

$$\Rightarrow \frac{di(0)}{dt} = -\frac{40}{3}$$

$$\Rightarrow A + B = 5$$

$$\left. \begin{array}{l} -\frac{8+2\sqrt{7}}{3}A + \frac{8-2\sqrt{7}}{3}B = -\frac{40}{3} \end{array} \right\} \Rightarrow \left\{ \begin{array}{l} A = \frac{5}{2} \\ B = \frac{5}{2} \end{array} \right.$$

Hence $i(t) = \frac{5}{2} \left[e^{\frac{-8+2\sqrt{7}}{3}t} + e^{\frac{-8-2\sqrt{7}}{3}t} \right] A$ for $t > 0$.

△注：若答案正确，给满分；若有错，给少分。（含卷）