

VE215 2022Fall Assignment 6

Due Date: 23:59, December 5th, 2022


In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

Exercise 6.1 (40%)

(a) For the given circuit, please calculate the total apparent power $|S|$, total real power P , total reactive power Q and the total power factor.

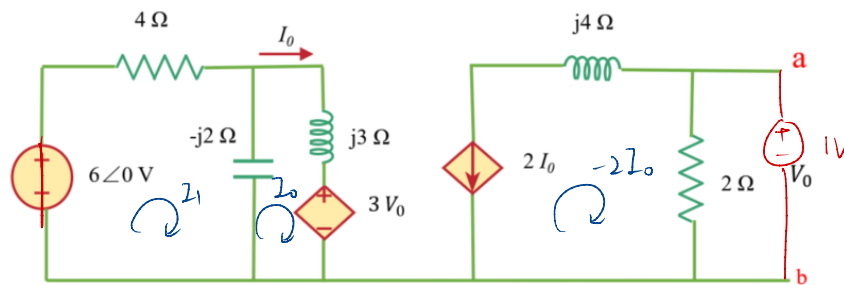(b) Suppose an impedance load Z_L is connected between a and b. Please calculate the value of Z_L that will absorb the maximum power and the value of that maximum power if

- Z_L is an impedance load
- Z_L is a pure resistance load



(a)

$$\begin{cases} -6\angle 0 + 4I_1 - j2 \cdot (I_1 - I_0) = 0 \\ -j2(I_0 - I_1) + j3I_0 + 3V_0 = 0 \\ V_0 = -4I_0 \end{cases}$$

(one right equation 5', all right 10')

$$\Rightarrow \begin{cases} I_0 = -0.132 + 0.198j & (2') \\ I_1 = 1.253 + 0.692j & (2') \\ V_0 = 0.527 - 0.791j & (2') \end{cases}$$

$$\begin{aligned} S &= I_1^2 \cdot 4 + (I_1 - I_0)^2 \cdot (-j2) + I_0^2 \cdot j3 + (-2I_0)^2 \cdot j4 + (-2I_0)^2 \cdot 2 \\ &= 8.649 - 3.249j \\ &= 9.239 \angle -20.587^\circ \end{aligned}$$

$$|S| = 9.239 \quad (1')$$

$$P = 8.649 \quad (1')$$

$$Q = -3.249 \quad (1')$$

$$\text{pf} = \cos(-20.587^\circ) = 0.934 \quad (1')$$

$$(b) \quad V_{Th} = V_0 = 0.527 - 0.791j \quad (5')$$

Z_{Th} :

$$4I_1 - j2(I_1 - I_0) = 0 \quad (2')$$

$$\begin{cases} -j2(I_0 - I_1) + j3I_0 + 3V_0 = 0 & (2') \\ V_0 = 1 \end{cases}$$

$$\Rightarrow \begin{cases} I_0 = -0.923 + 1.615j & (1') \\ I_1 = 0.462 + 0.692j & (1') \end{cases}$$

$$Z_{Th} = \frac{1}{2I_0 + V_0/2} = -0.110 - 0.264j \quad (2')$$

Impedance load:

$$Z_L = Z_{Th}^* = -0.110 + 0.264j \quad (2')$$

$$R_{Th} < 0, \quad P_m = \infty / -2.05 \text{ W} \quad (1')$$

Resistive load:


$$Z_L = \sqrt{0.110^2 + 0.264^2} = \frac{2}{7} \Omega \quad (2')$$

$$P_m = \frac{V_{Th}^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} = 2.57 \text{ W} \quad (1')$$

VE215 2022Fall Assignment 6

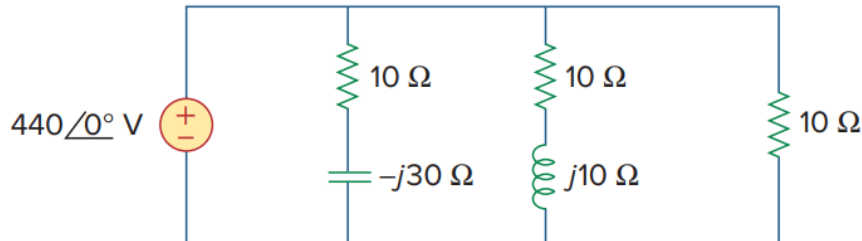Exercise 6.2 (30%) Consider the power system shown below. Calculate:

- the total complex power
- the power factor
- the parallel capacitance necessary to establish a unity power factor



$$\begin{aligned}
 (a) \quad S &= \frac{440^2}{(10 - j30)^*} + \frac{440^2}{(10 + j10)^*} + \frac{440^2}{10} \quad (5') \\
 &= 30976 + 3872j \quad (5')
 \end{aligned}$$


$$\begin{aligned}
 (b) \quad \theta &= \tan^{-1} \left(\frac{3872}{30976} \right) = 7.125 \quad (5') \\
 \text{pf} &= \cos \theta = 0.992 \quad \text{lagging} \quad (5')
 \end{aligned}$$

$$\begin{aligned}
 (c) \quad P &= 30976 \text{ W} \\
 C &= \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{\text{rms}}^2} \quad (5') \\
 &= \frac{30976 \cdot \tan(7.125)}{1000 \cdot 440^2} \\
 &= 2 \times 10^{-5} \text{ F} / \frac{1}{50} \text{ W F} \quad (5')
 \end{aligned}$$

VE215 2022Fall Assignment 6

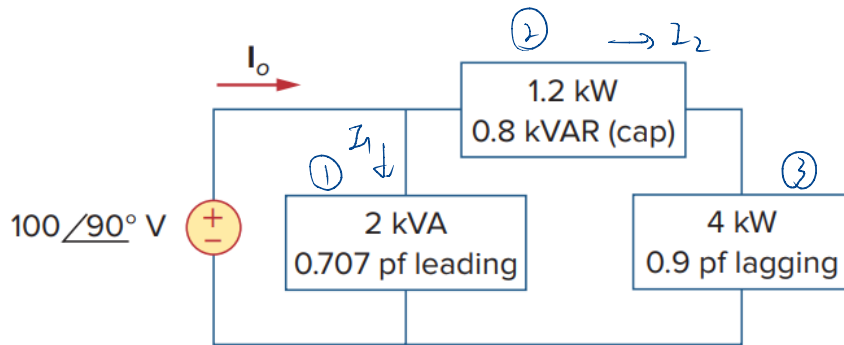Exercise 6.3 (30%)

Given the circuit below, calculate the equivalent impedance in each of the blocks. Also find I_o and the overall complex power supplied.



$$S_1 = 1.414 - 1.414j \text{ kVA} \quad (2')$$

$$S_2 = 1.2 - 0.8j \text{ kVA} \quad (2')$$

$$S_3 = 4 + j4 \tan(\cos^{-1}(0.9)) = 4 + 1.937j \text{ kVA} \quad (2')$$

$$I_1^* = \frac{S_1}{V} = \frac{1.414 - 1.414j}{j100} = -14.14 - 14.14j \text{ A} \Rightarrow I_1 = -14.14 + 14.14j \quad (2')$$

$$I_2^* = \frac{S_2 + S_3}{V} = 11.37 - 5.2j \text{ A} \Rightarrow I_2 = 11.37 + 5.2j \quad (2')$$

$$I_o = I_1 + I_2 = -2.77 + 66.14j = 66.198 \angle 92.398^\circ \text{ A} \quad (4')$$

$$S = S_1 + S_2 + S_3 = 6.614 - 0.277j \text{ kVA} \quad (4')$$

$$Z_1 = \frac{V}{I_1} = 3.54 - 3.54j = 5 \angle -45^\circ \Omega \quad (4')$$

$$Z_2 = \frac{S_2}{|I_2|^2} = 0.424 - 0.282j = 0.509 \angle -33.69^\circ \Omega \quad (4')$$

$$Z_3 = \frac{S_3}{|I_2|^2} = 1.412 + 0.684j = 1.569 \angle 25.839^\circ \Omega \quad (4')$$